The Wiring diagram of 4 channel Relay with Pi

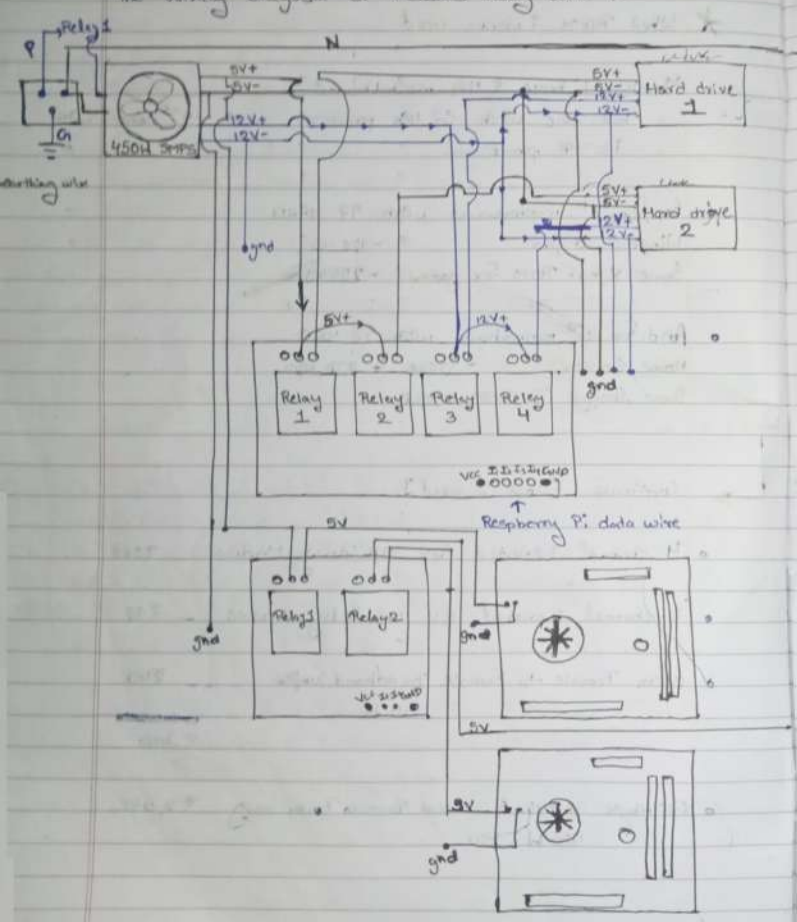

Power diagram

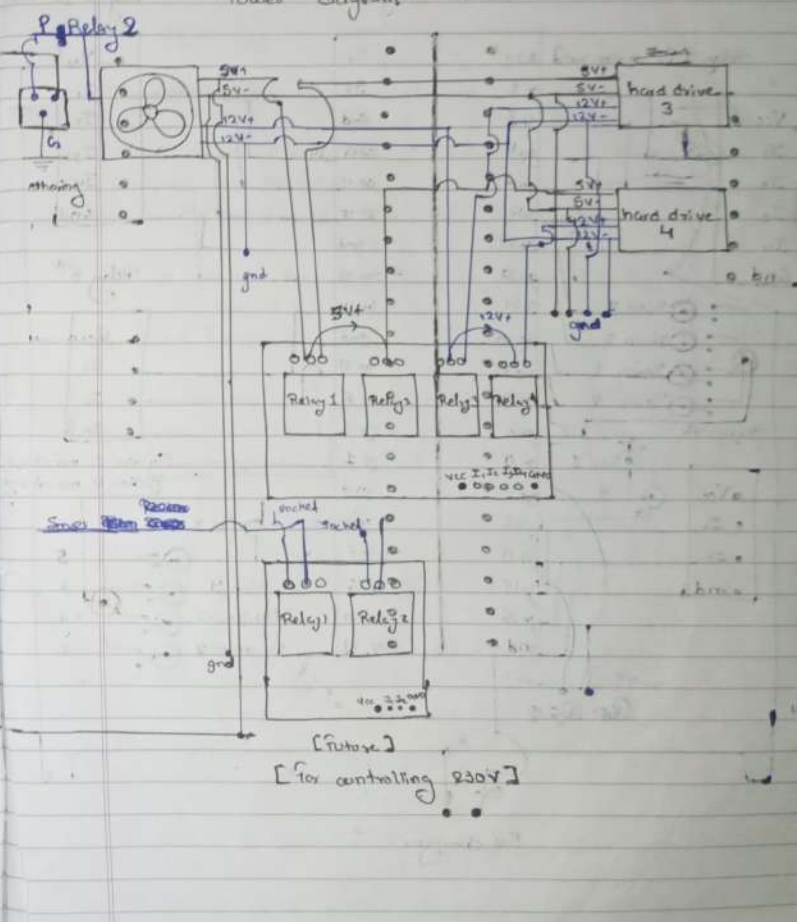

[future]

[for controlling 230V]

Control diagram

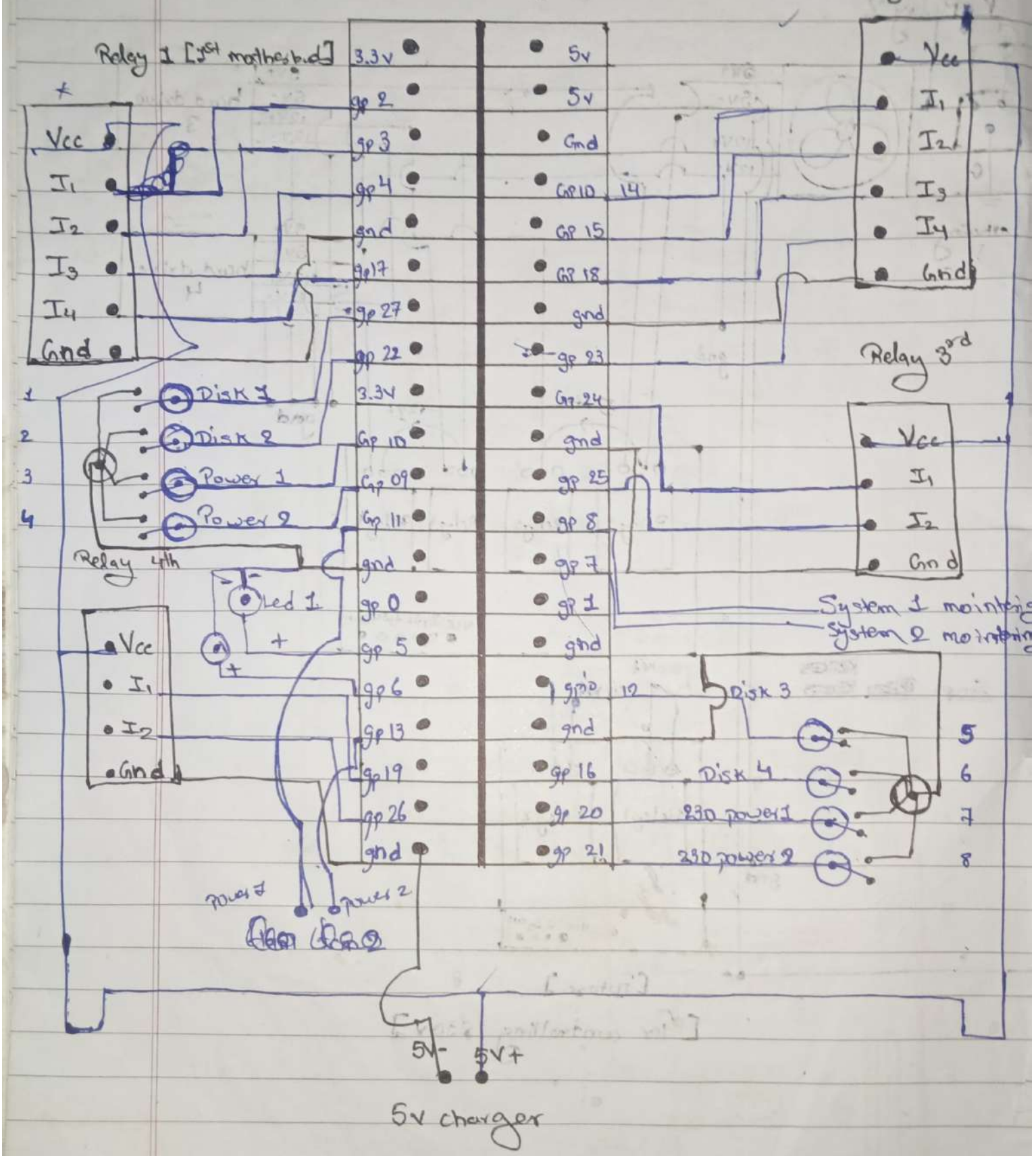

Page No.:
Date: / /

★ What philosophy are used here.

For Local Mode

- If we pressed the switch 1, Relay 1 and Relay 3 are going to NO → NC. and hardrive 1 will be Ready to used [motherboard 1]

- If we pressed the switch 2, Relay 2 and Relay 4 are going to NO → NC and harddrive 2 will be Ready to used. [motherboard 1]

- If we pressed the switch 5, Relay 1 and Relay 3 are going to NO → NC and hardrive 3 will be Ready to used [motherboard 2]

- If we pressed the switch 6, Relay 2 and Relay 4 are going to NO → NC and hardrive 4 will be Ready to used [motherboard 2]

- If drive 1 is ready to used drive 2 relays will be NO if NC else as it is.

- If drive 2 is ready to used drive 1 relays will be NO if NC else as it is.

- If switch 3 is pressed, Motherboard 1 will be ON

- If switch 4 is pressed, Motherboard 2 will be ON.

Teacher's Signature:

Page No.:
Date: / /

- Web app test simple

Start with Relay 1 [Two channel Relay]
Web interface has two button
system 1 and system 2

System 1 and system 2 ax in Red colour button
When we pressed the system 1 or system 2 button
colour change to green and In ~~behind~~ below the
system "online" text is written.

System 1 triger the gpio 19 so the relay 1 is Ready
and new interface open in web page.

System 2 trigger then gpio 26 so the relay 2 is Ready
and new interface open in web page

both the interface is different system 1 open different webpage
and system 2 open different web page.

When I pressed the physical switch it ~~triggers~~ that
was connected on gpio 10 and gnd it triggers the
relay 1 and all the same thing also shown in webpage
colour change Red to green and open new interface
(If we check the web page otherwise) just green button
and below that online text

Teacher's Signature:

Page No.:
Date: / /

Relay Setup

Relay	GPIO pin	Description
R1	Gpio 19	System 1 [2 channel relay 1]
R2	Gpio 26	System 2 [2-channel relay 2]
R3	Gpio 2	1st -4 channel relay IN1
R4	Gpio 3	1st 4-channel relay IN2
R5	Gpio 4	1st-4-channel relay IN3
R6	Gpio 17	1st-4-channel relay IN4
R7	Gpio 14	2nd-4-channel relay IN1
R8	Gpio 15	2nd-4-channel relay IN2
R9	Gpio 18	2nd-4-channel relay IN3
R10	Gpio 23	2nd-4-channel relay IN4
R11	Gpio 24	2nd-2-channel relay IN1
R12	Gpio 25	2nd-2-channel relay IN2

Manual Pushbutton Inputs

Button	GPIO Pin	Description	
SW1	Gpio 27	System 1	R1
SW2	Gpio 22	System 2	R2
SW3	Gpio 10	Disk 1	R3 + R5
SW4	Gpio 9	Disk 2	R4 + R6
SW5	Gpio 12	Disk 3	R7 + R9
SW6	Gpio 16	Disk 4	R8 + R10
SW7	Gpio 20	Power 1	R11
SW8	Gpio 21	Power 2	R12

Teacher's Signature:

System 1 (Outgoing cable)

System 2 (Outgoing cable)

Base (Outgoing cable)

PROJECT ZERO
DOMINUS
Made with Chat gpt

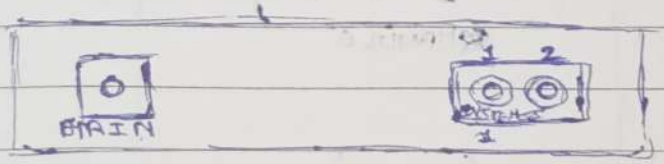
MAIN
1
2

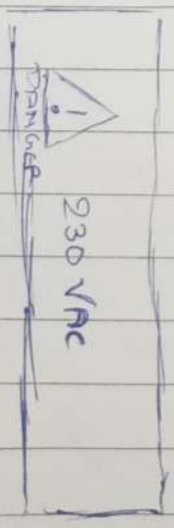
DANGER
230 VAC

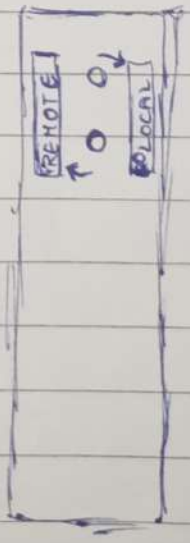
REMOTE
LOCAL

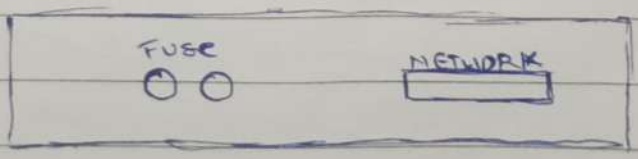
FUSE
NETWORK

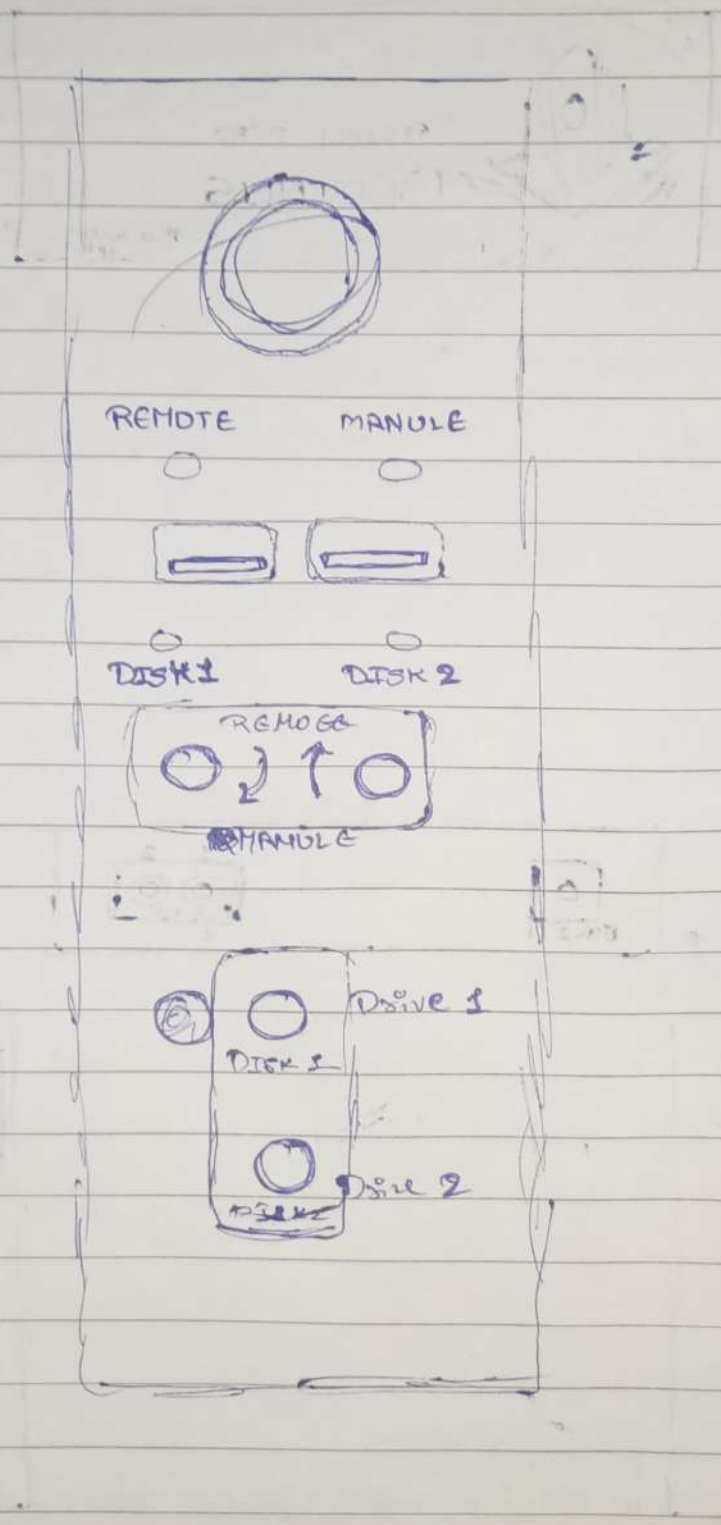
REMOTE
MANULE
DISK 1
DISK 2
REMOTE
MANULE
Drive 1
DISK 1
Drive 2

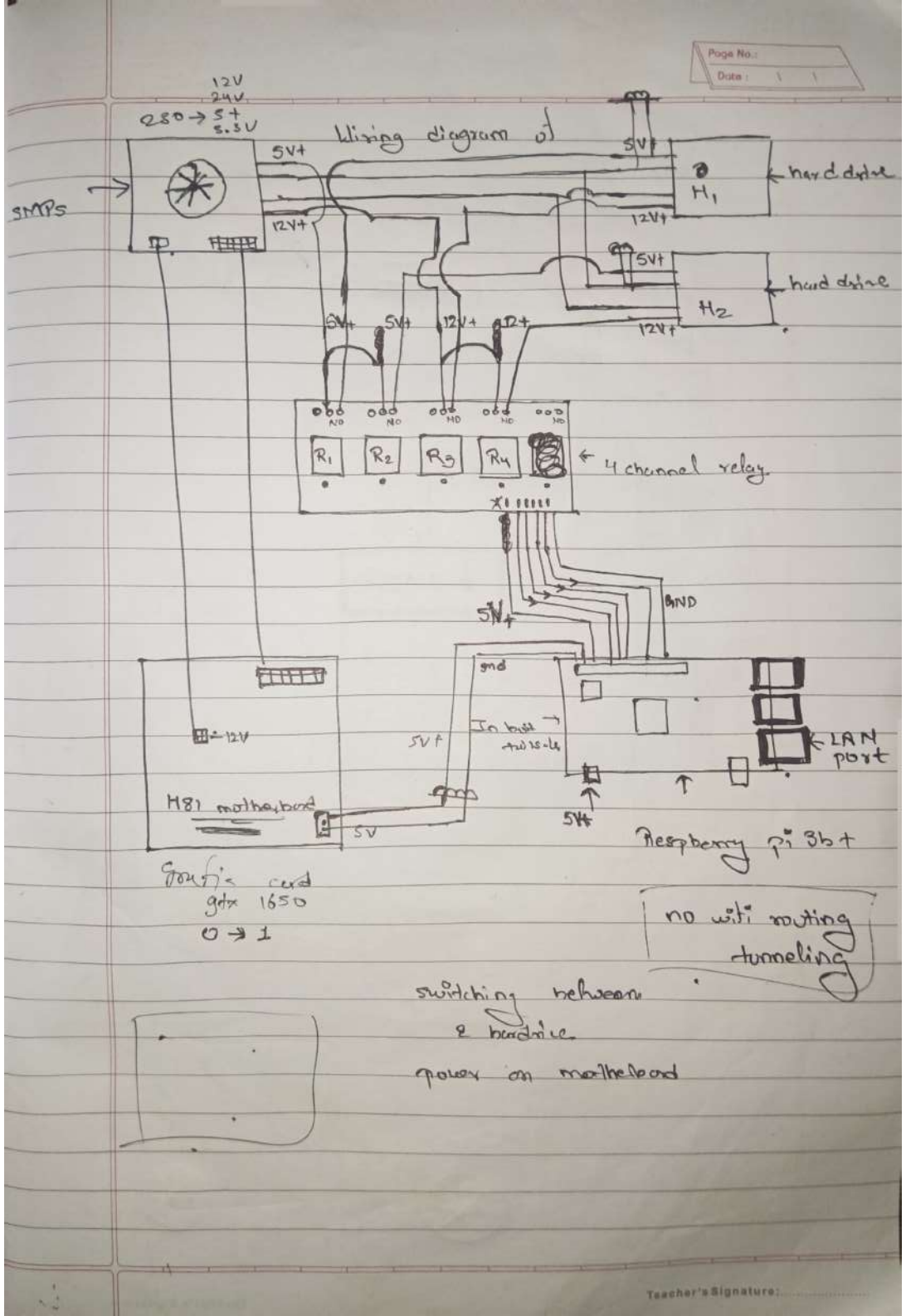
Page No.:
Date: / /
Wiring diagram of
SMPS
12V
24V
280 → 5+
5.3V
5V+
12V+
H1
hard drive
H2
hard drive
5V+
12V+
NO
R1
R2
R3
R4
4 channel relay
GND
5V+
gnd
5V+
12V
H81 motherboard
5V
LAN port
Raspberry pi 3b+
Graphic card
gtx 1650
0 → 1
no wifi routing
tunneling
switching between
2 hardrive
power on motherboard
Teacher's Signature:

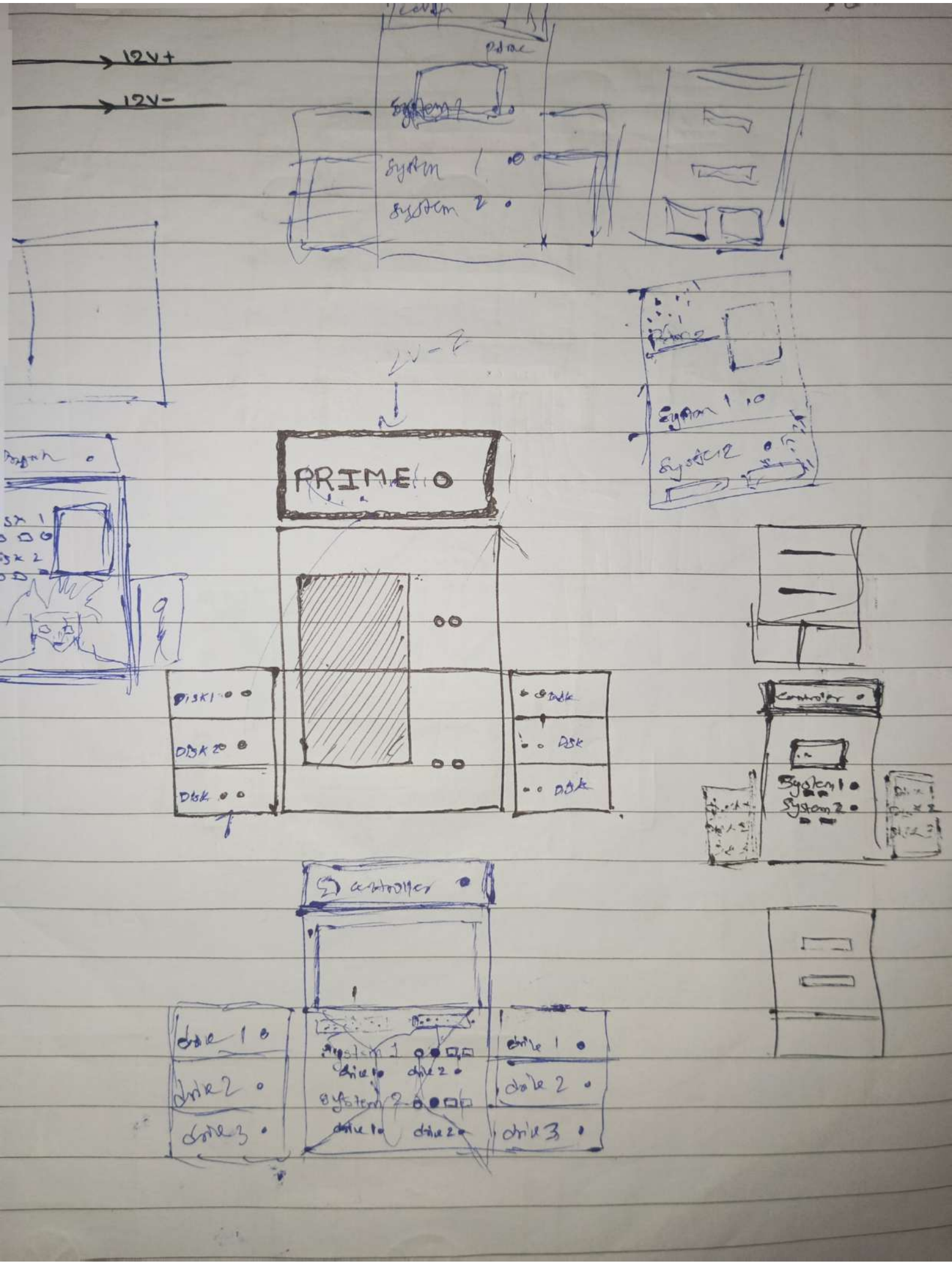
12V+
12V-
System 1
System 2
PRIME
DISK 1
DISK 2
Disk
Controller
System 1
System 2
drive 1
drive 2
drive 3

The skelton design

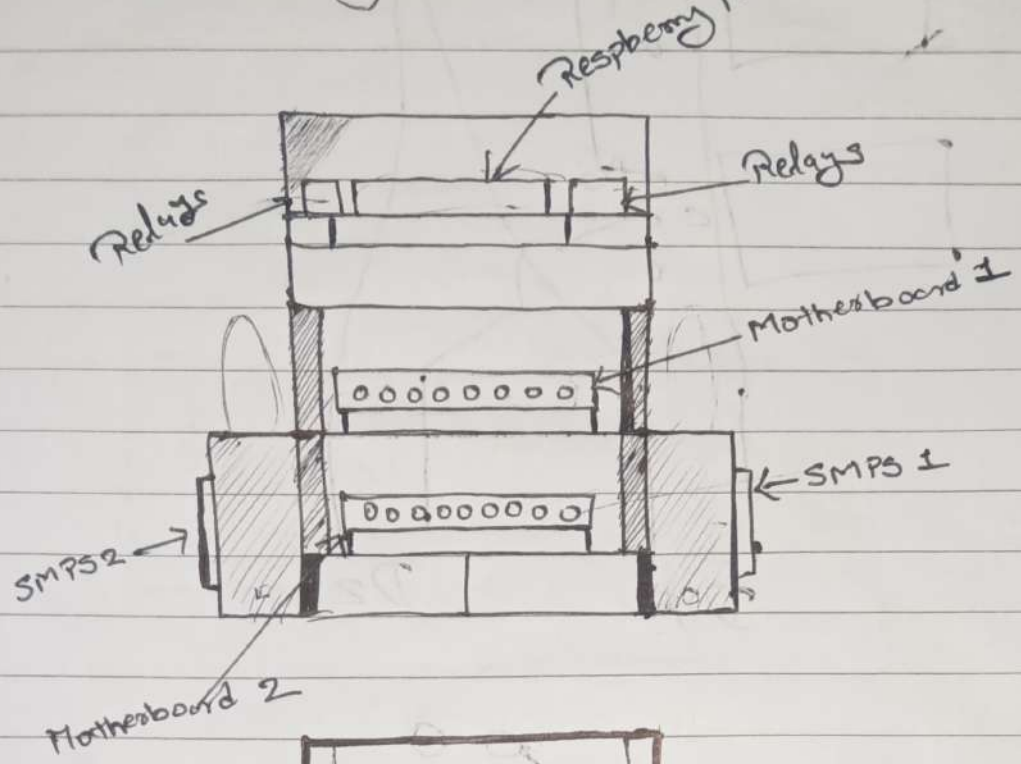

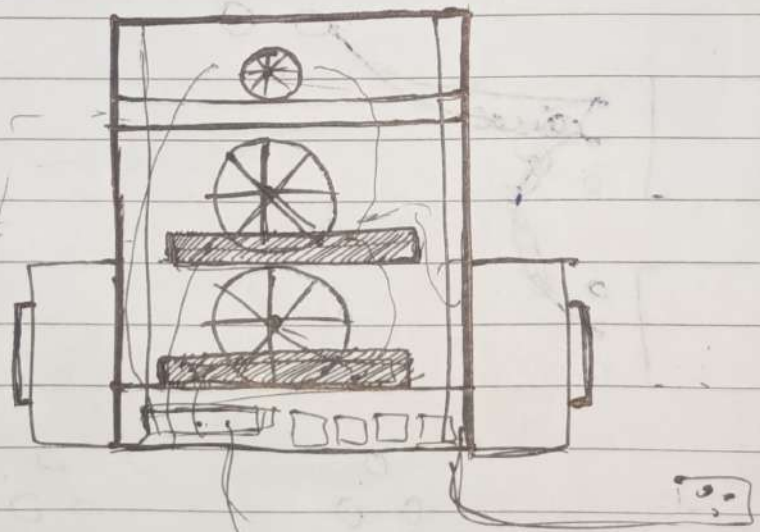

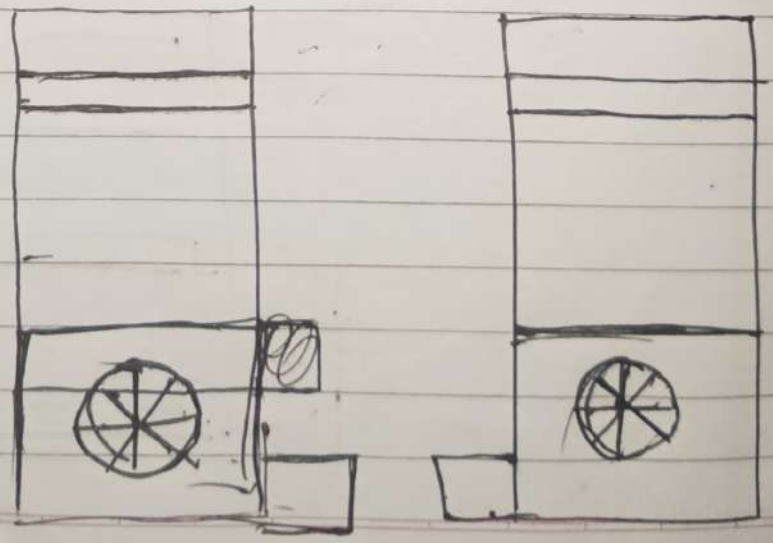

2+2 = Male 2
Female 2

= Female
= Male

16 = Female
16 = Male

8 = Connector F
8 = Connector M

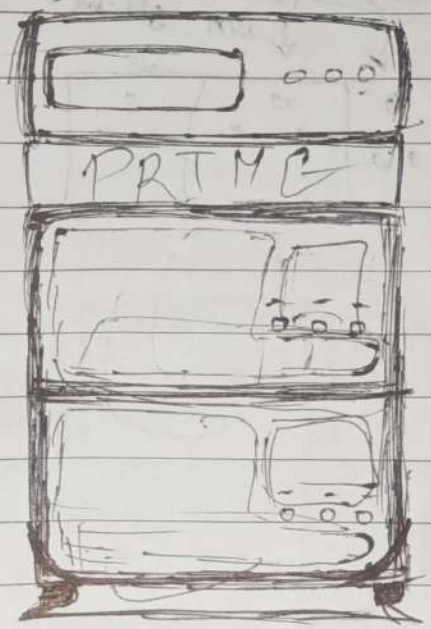

4 connector

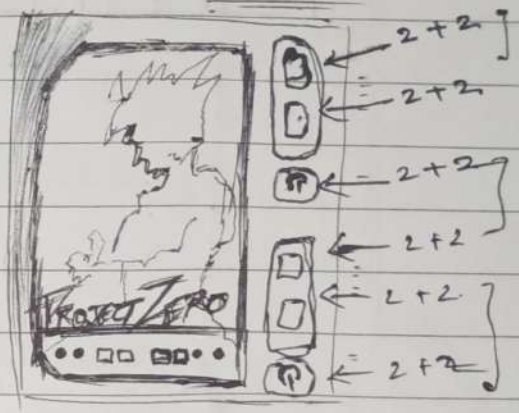

Top View

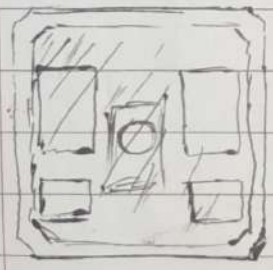

L Side View

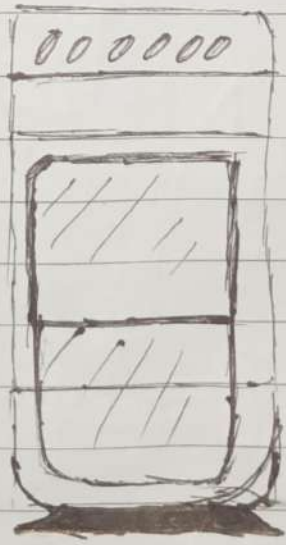

R Side View

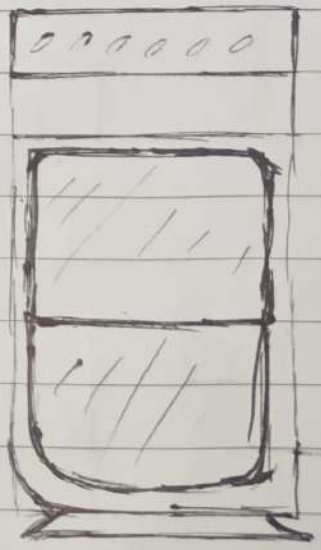

2+2
+
2+2

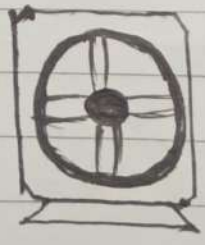

Front Panel

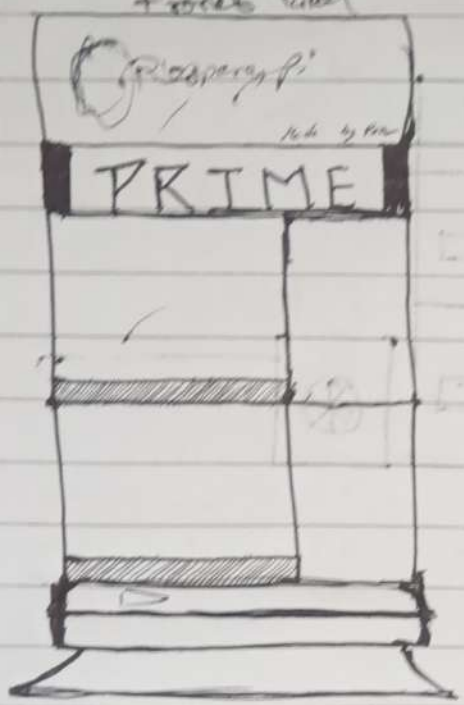

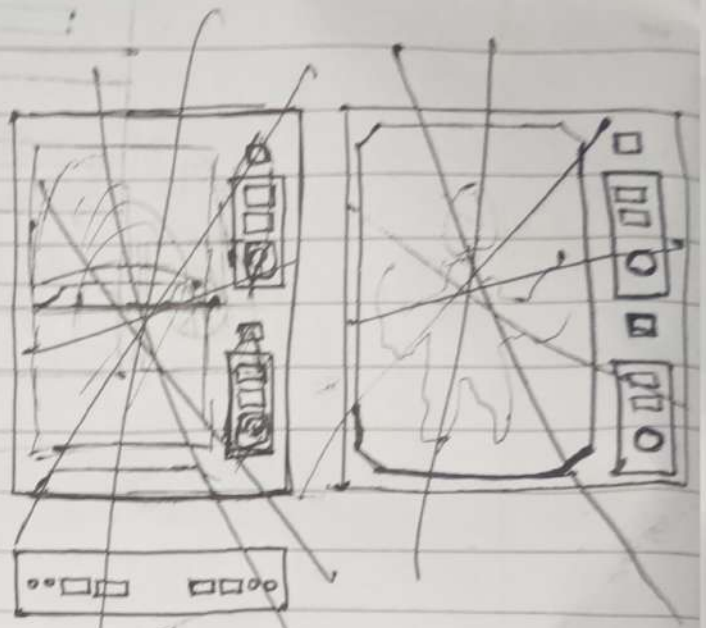

setelion

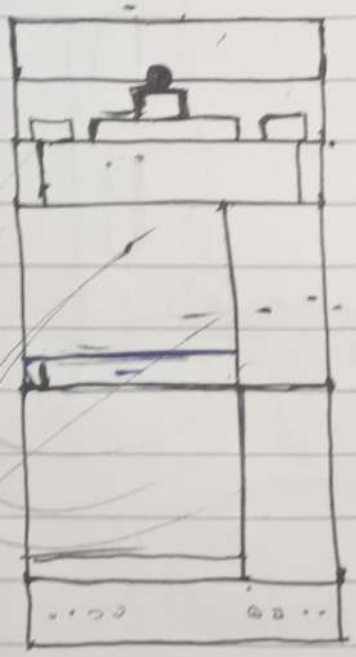

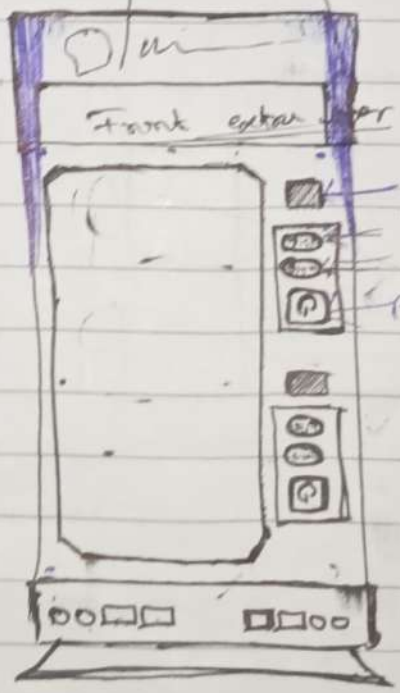

400mm

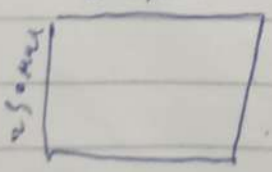

Teacher's Signature:

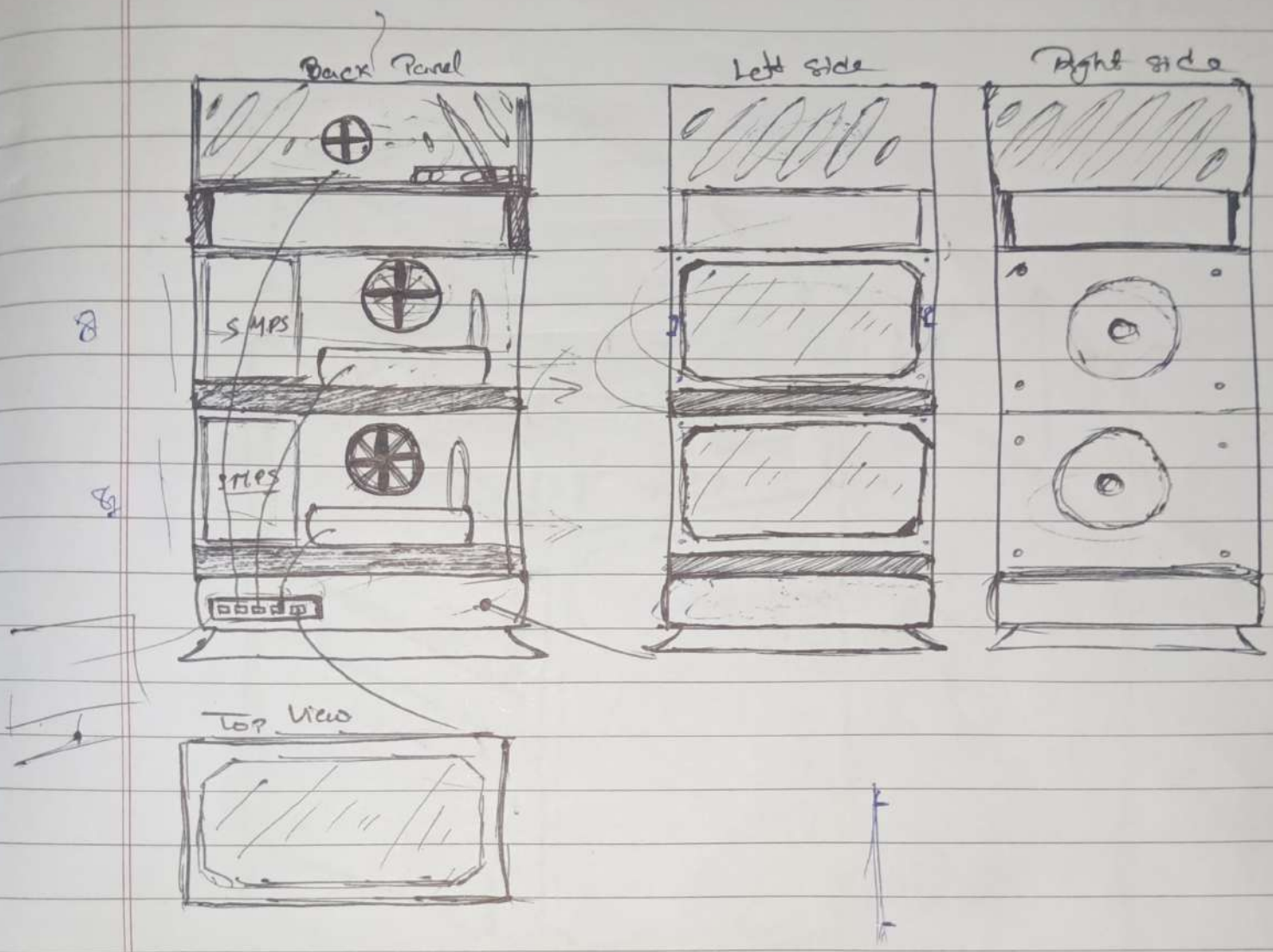

How to build this.

First I need to take the measurement of all things
Motherboards, SMPS, raspberry pi, relay.
Also I need to see the height so, Fan can be mount easily and look cool.

Void
Void
90 cm
35 cm

Page No.:
Date : / /

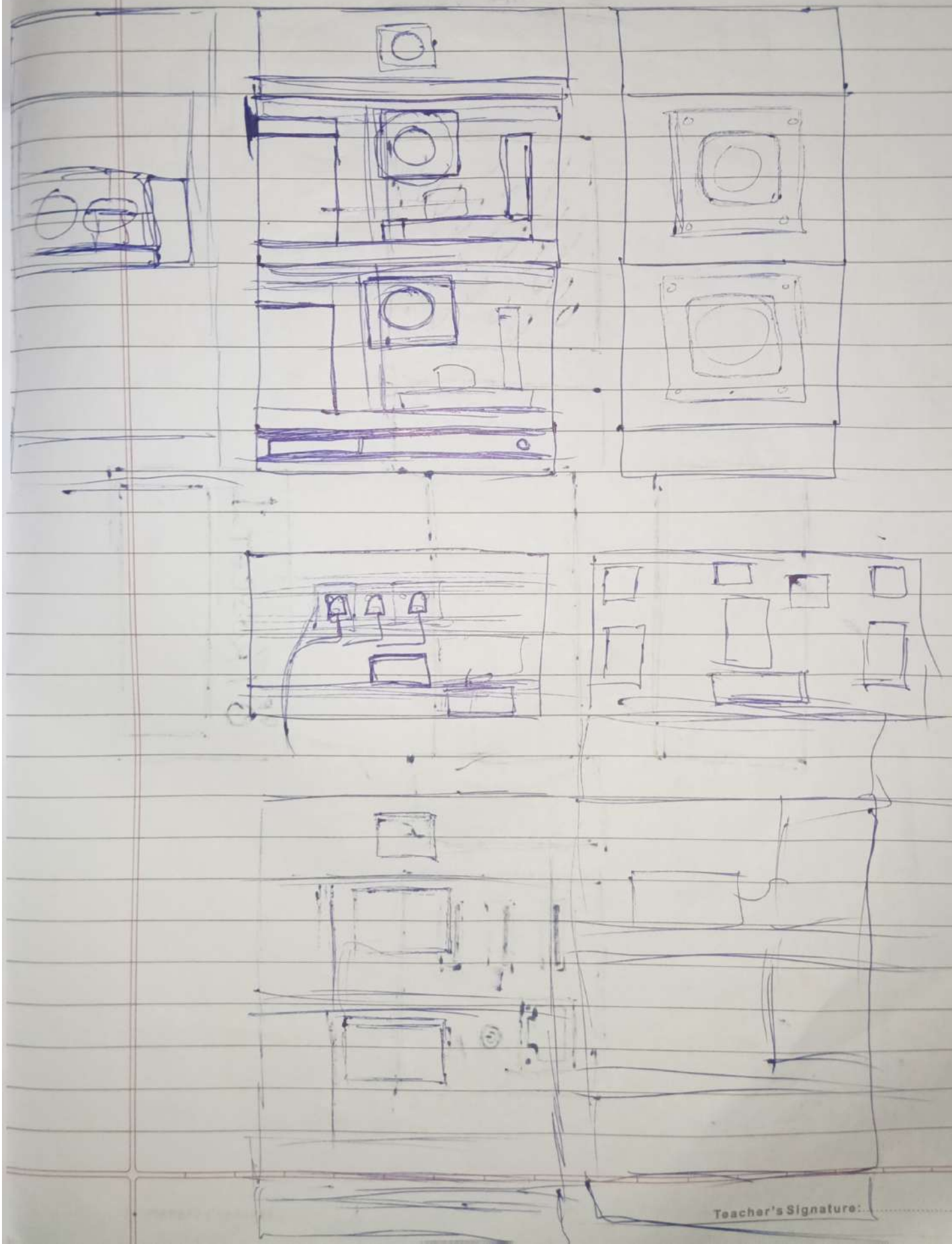

Teacher's Signature:

DATE : SUBJECT : PAGE :

- Connector For base

Adapter E-Switch

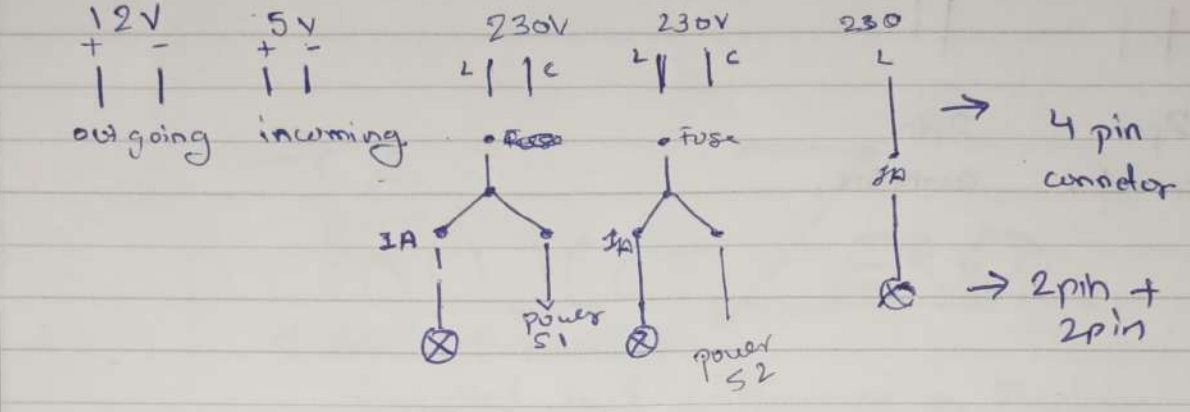

- Connector For system 2

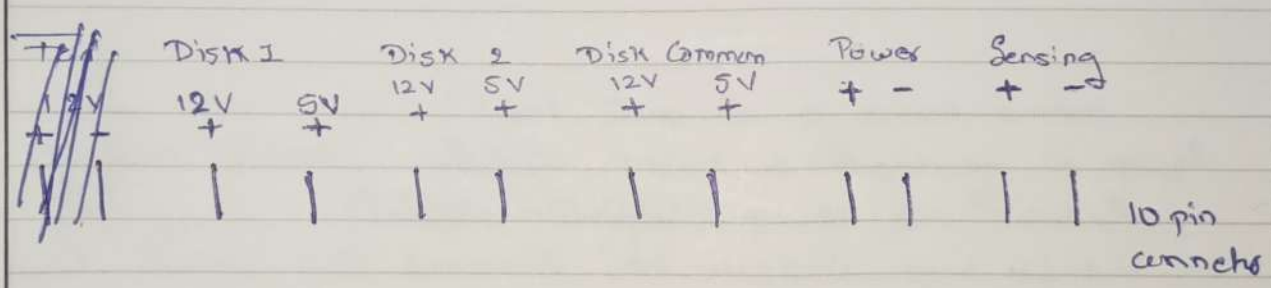

Switch.

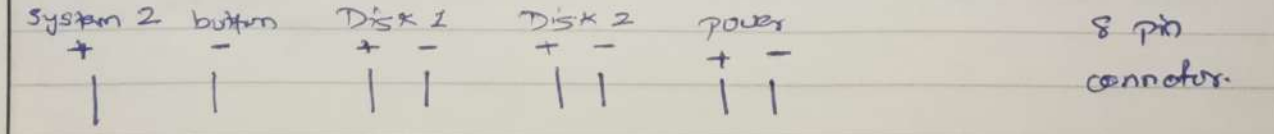

- Connector for system 1

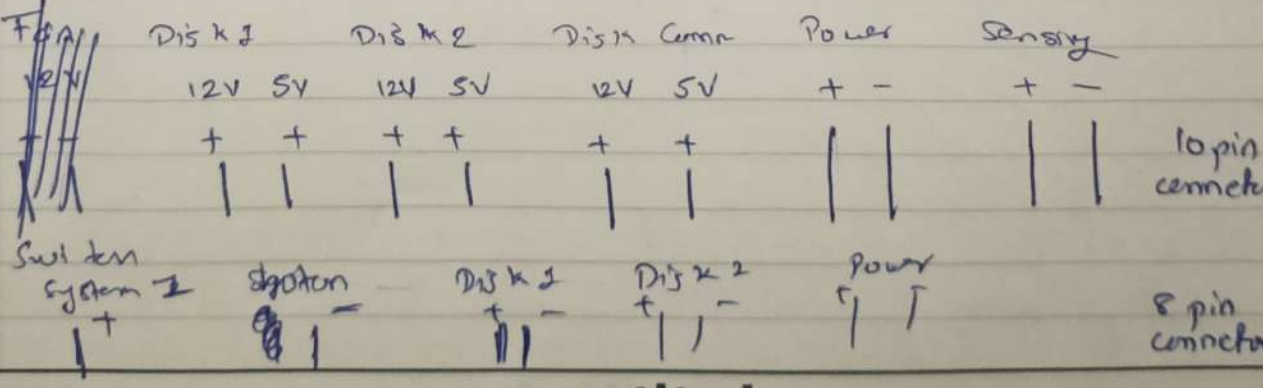

servilink

Base

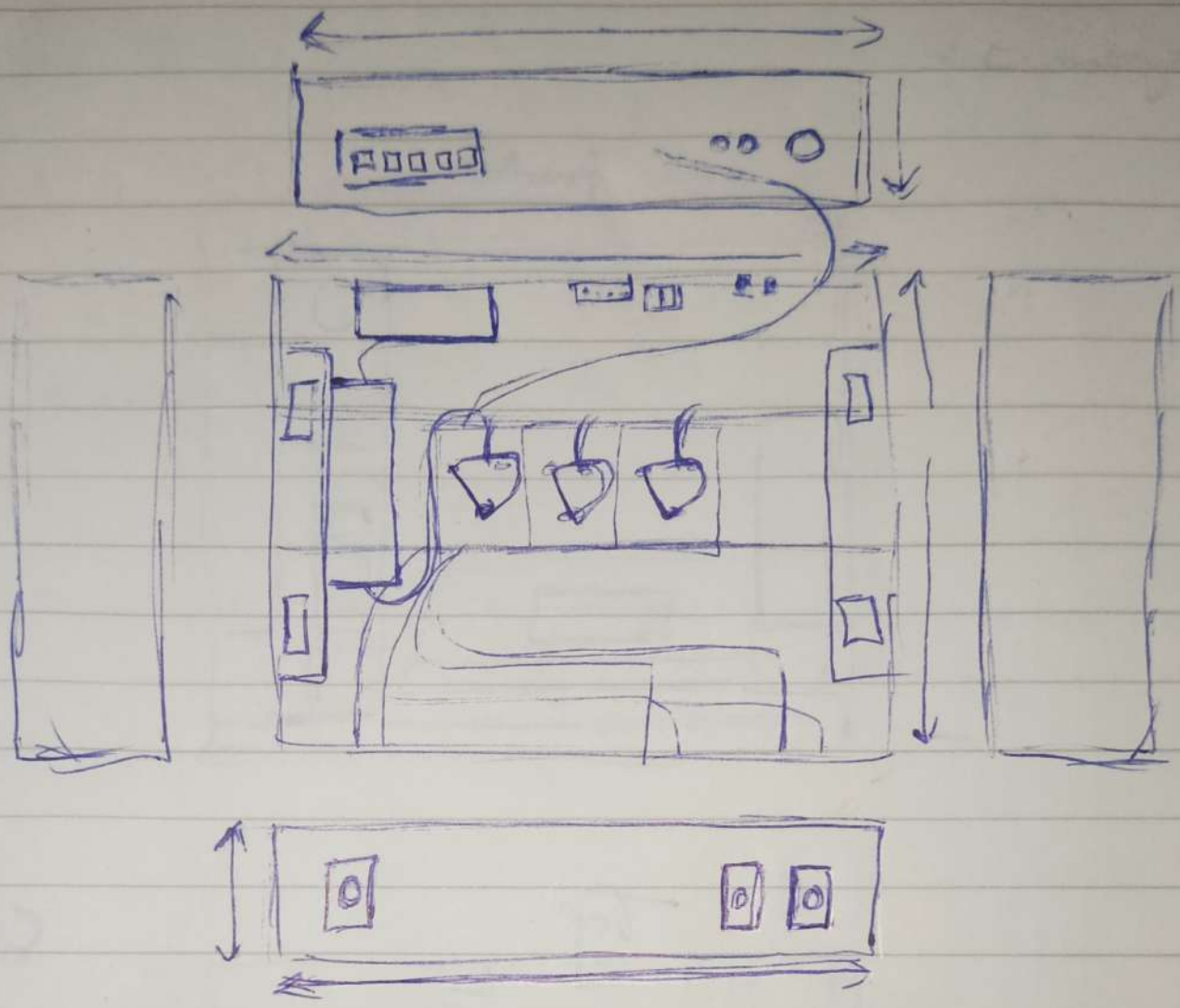

The Systems:

The system I :

front

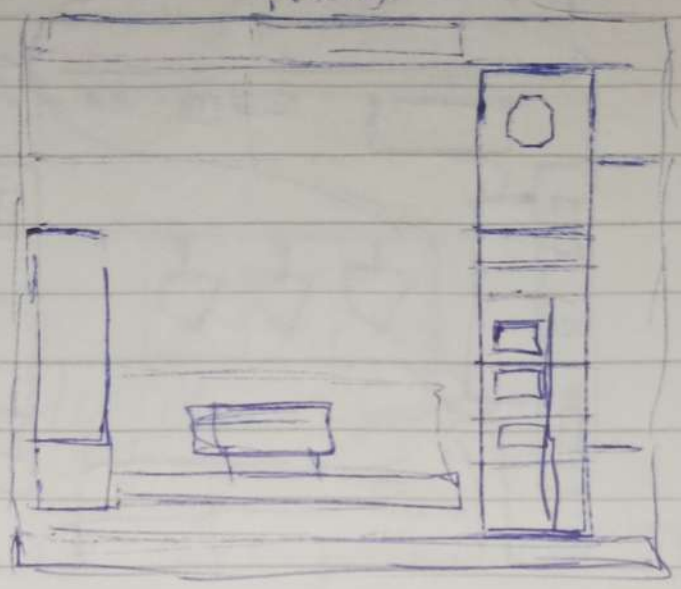

Top

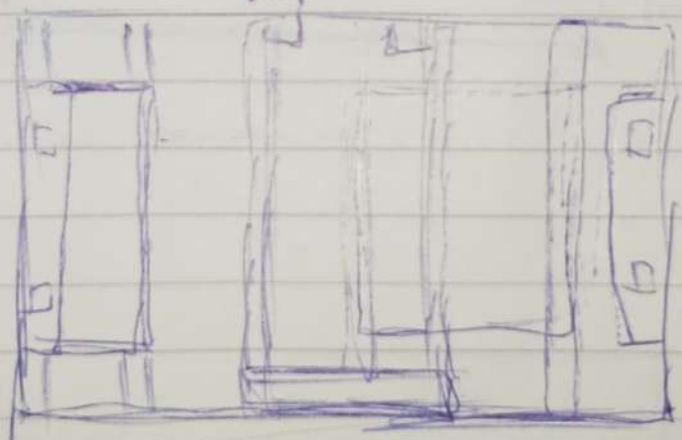

Side left

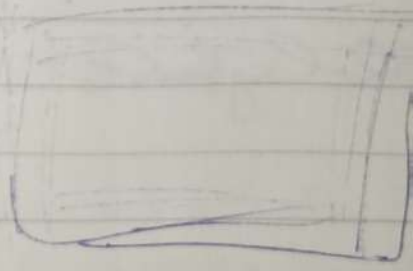

Side Right

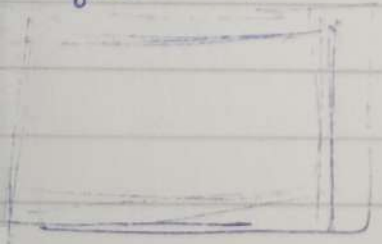

back

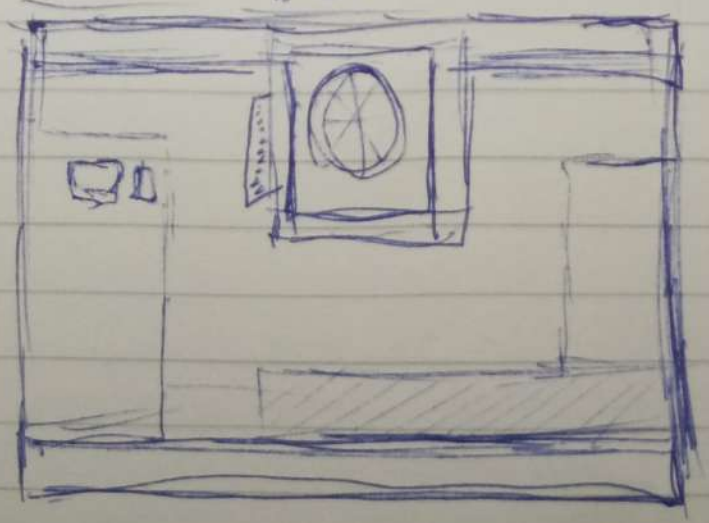

2 Controller

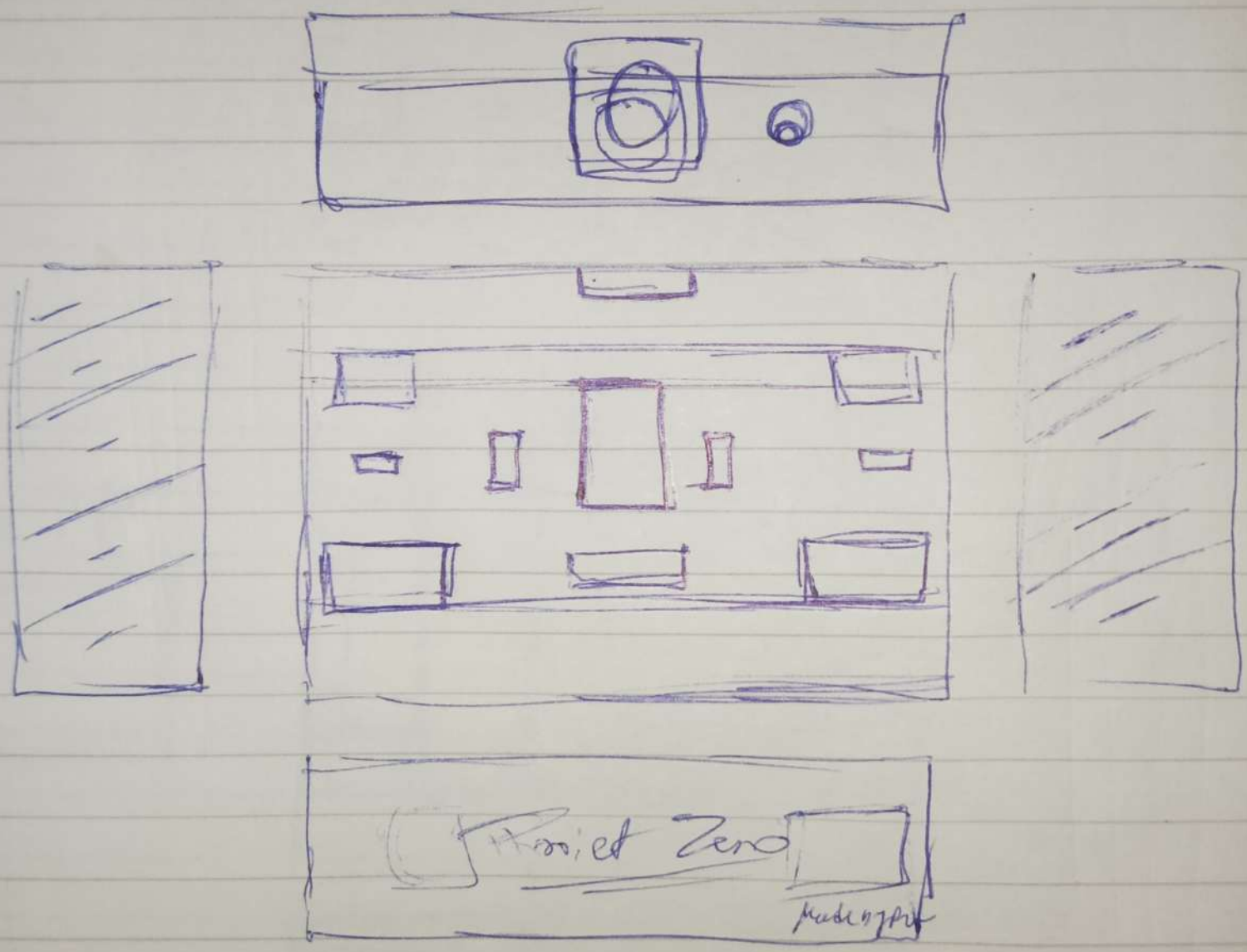

DATE : SUBJECT : PAGE :

Chapter 7 : The wiring diagram of Project 2000

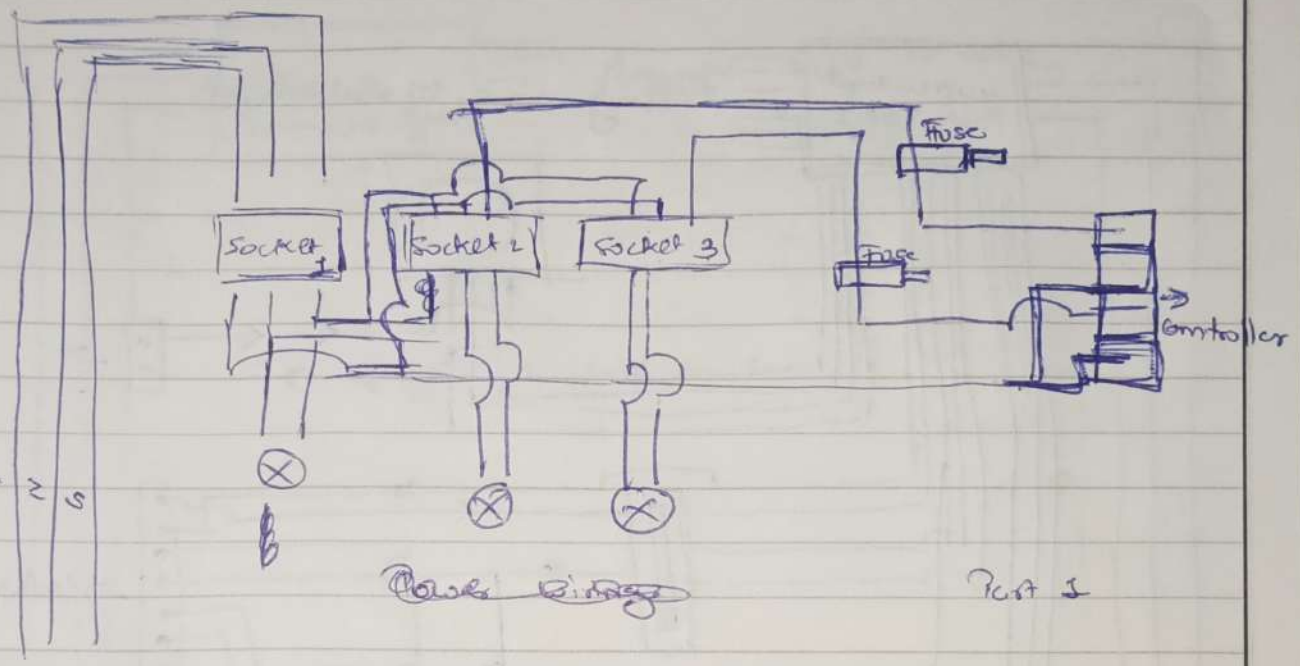

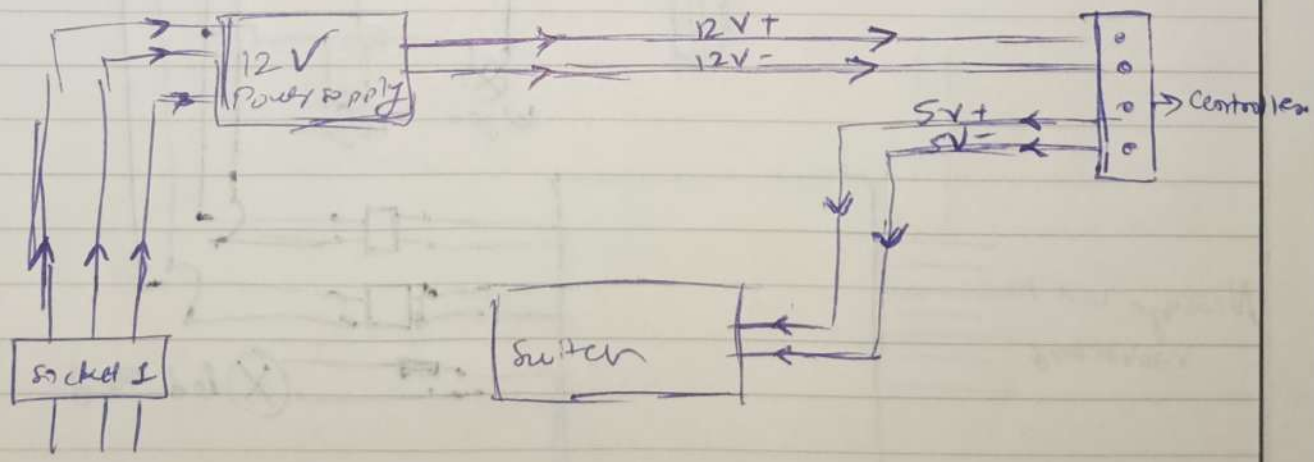

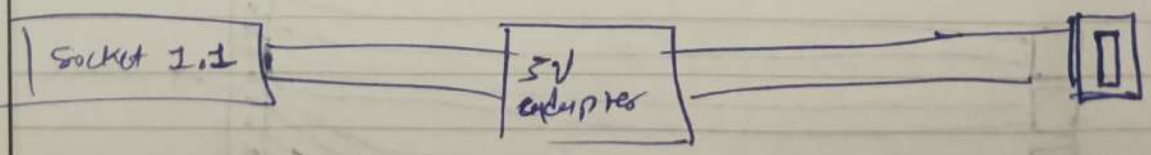

servilink

DATE : SUBJECT : PAGE :

The system 2

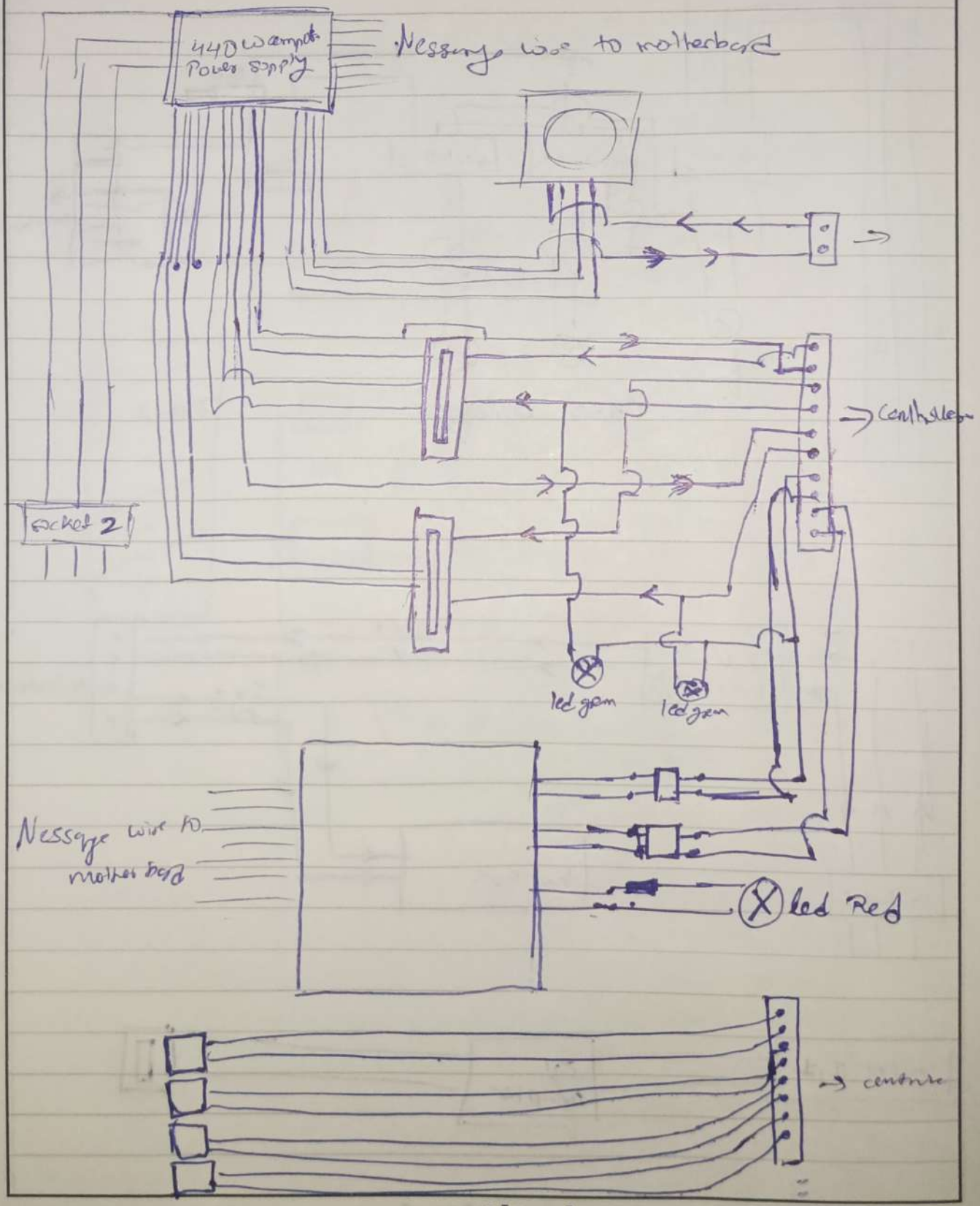

servilink

DATE : SUBJECT : PAGE :

The system 2

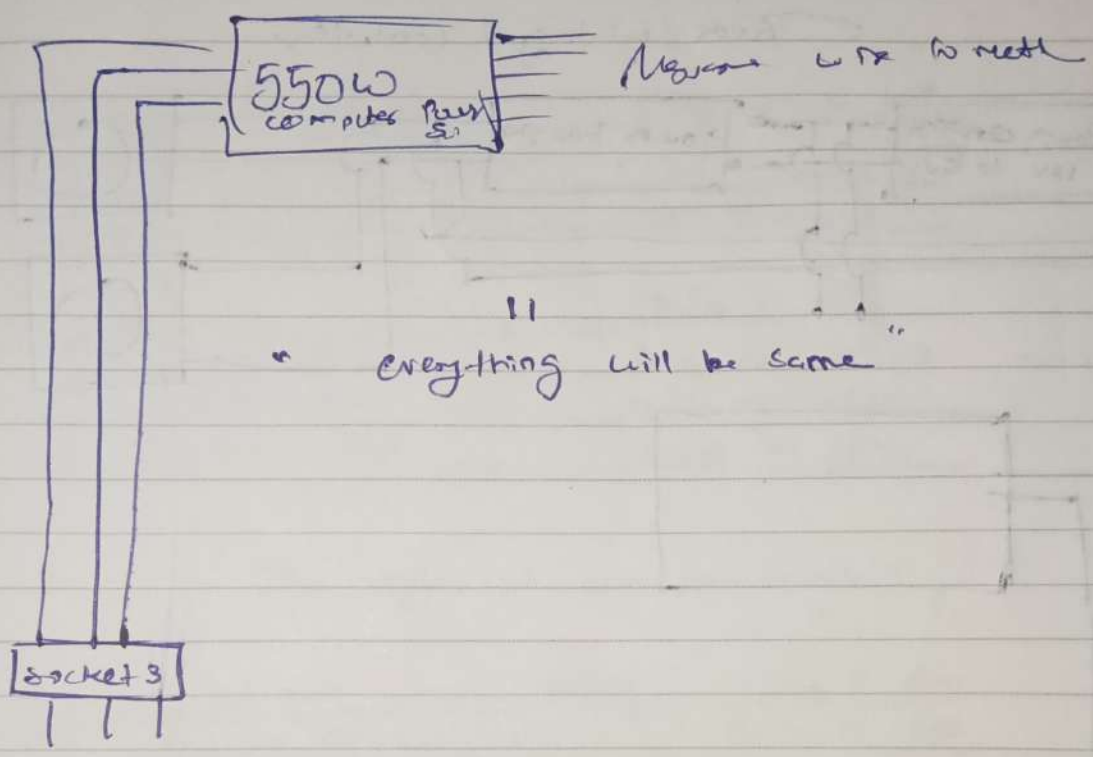

" " " everything will be same "

servilink

DATE : SUBJECT : PAGE :

The Controller wiring

Power wiring of Controller

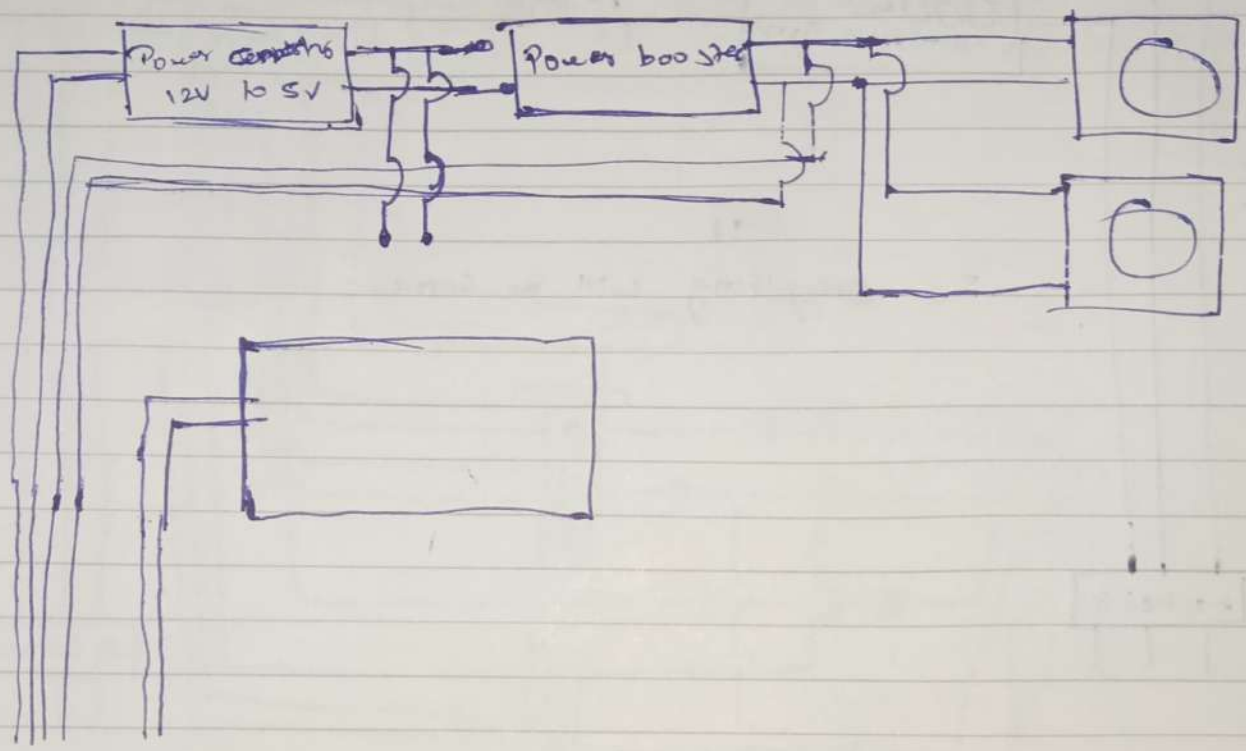

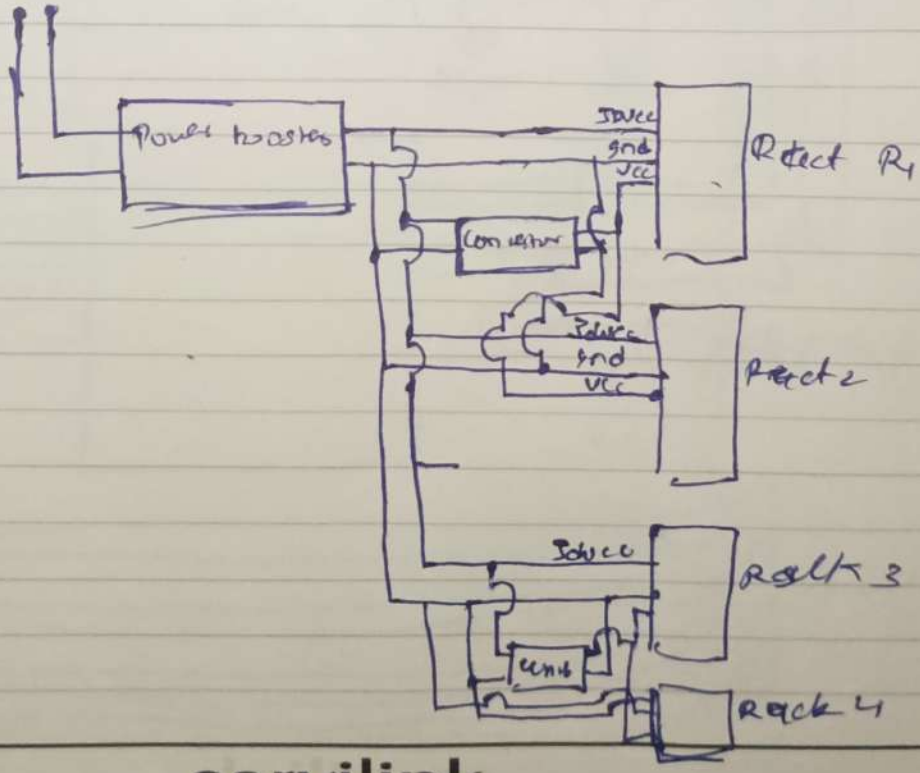

servilink

DATE : SUBJECT : PAGE :

The cables

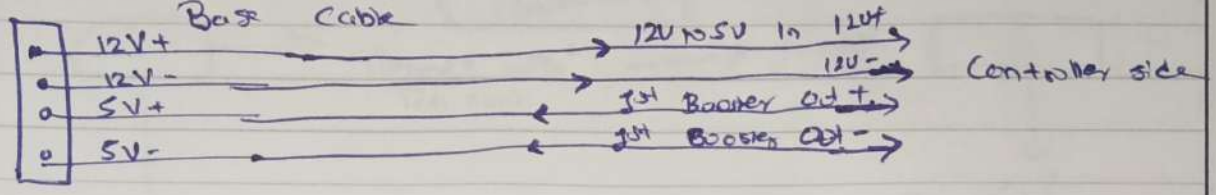

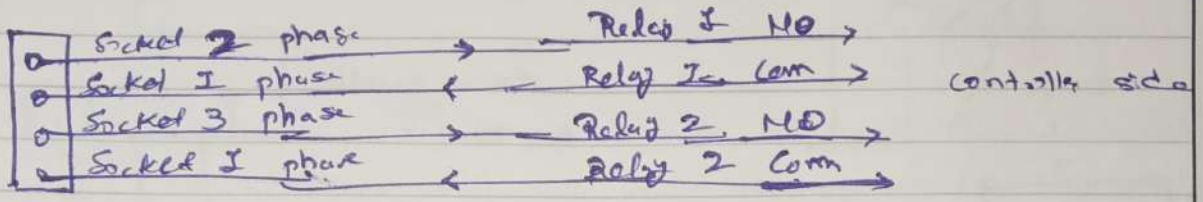

The system 1 and 2 cable

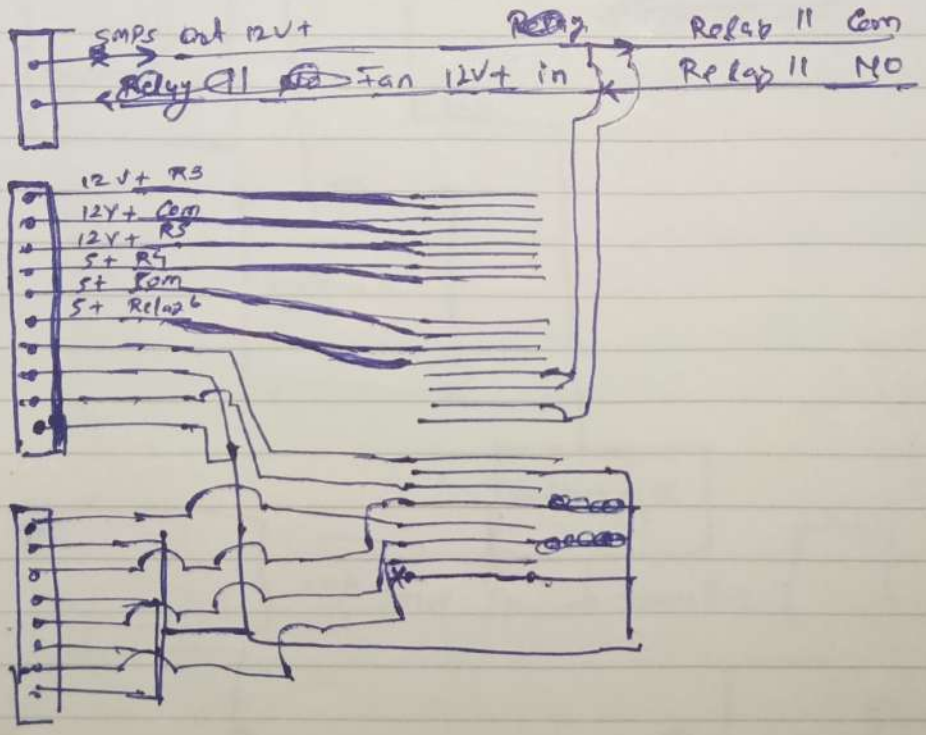

servilink

DATE : SUBJECT : PAGE :

Networking diagram

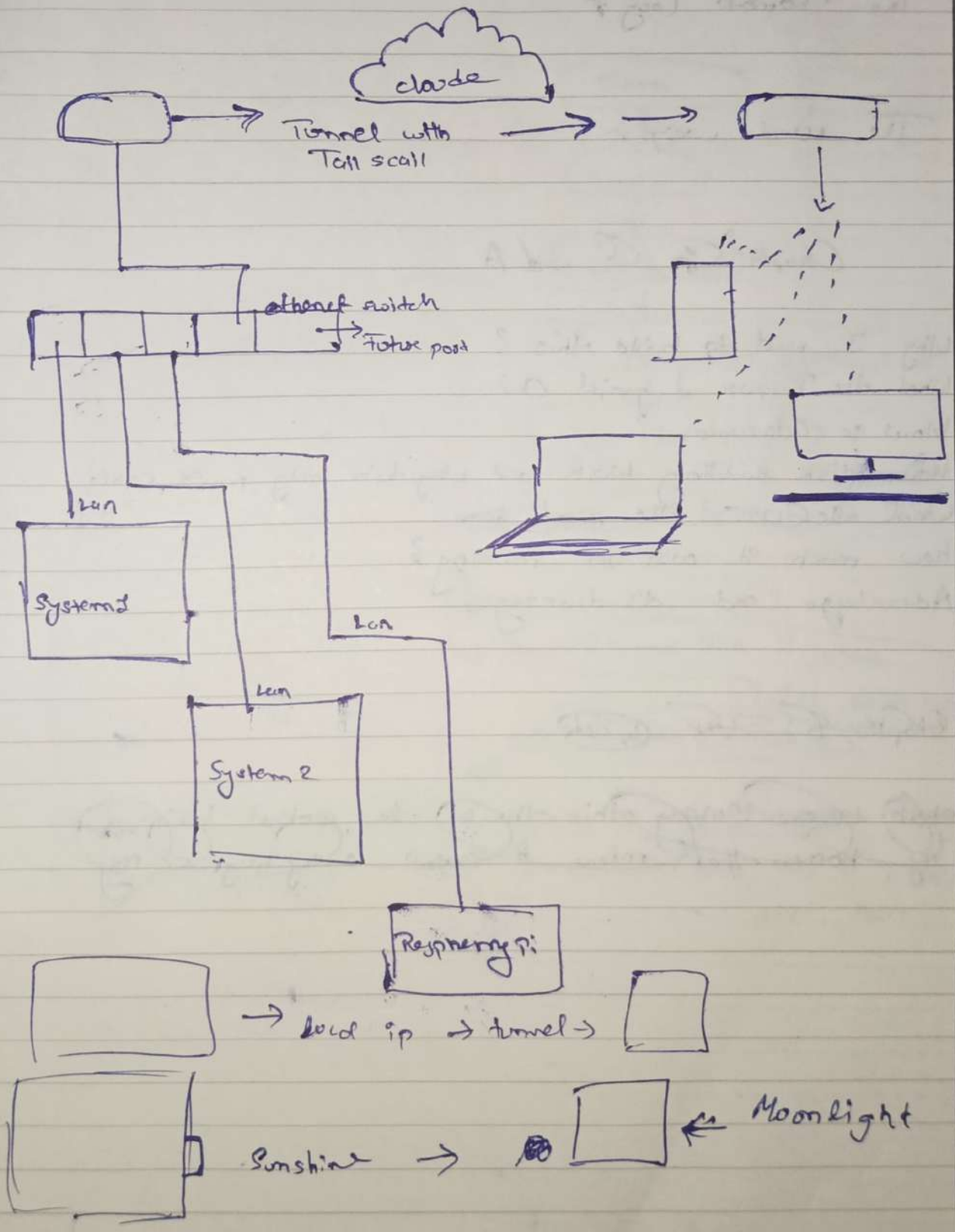

servilink

DATE : SUBJECT : PAGE :

- For Power switch

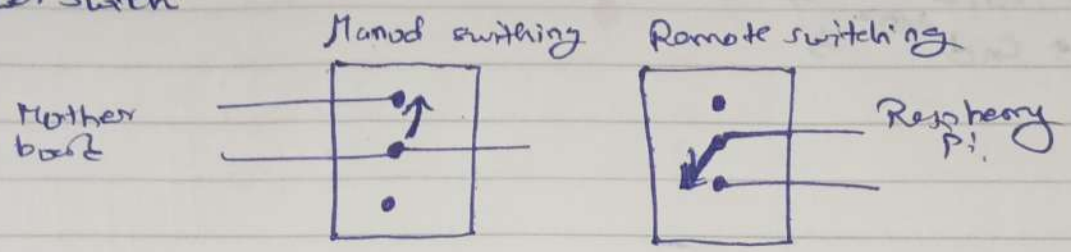

- For disk selection

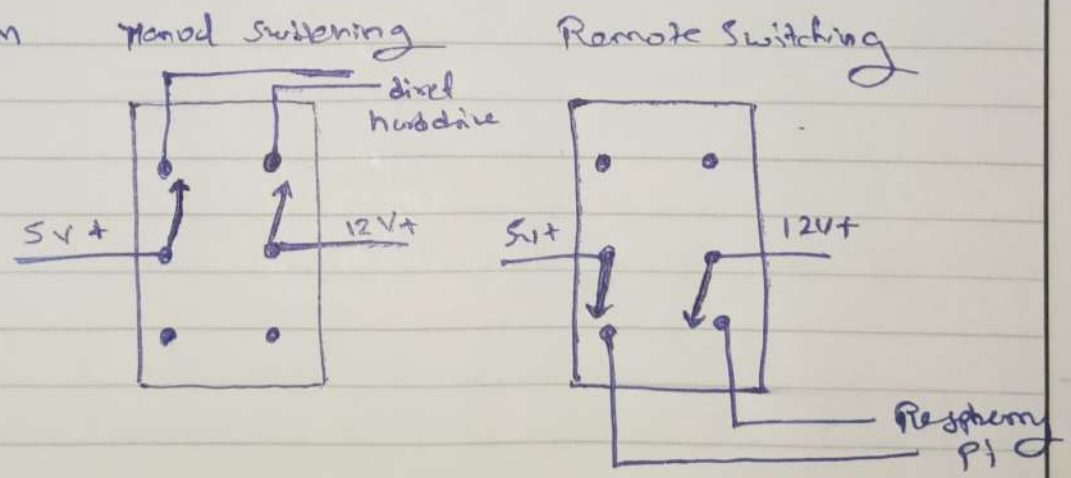

servilink